
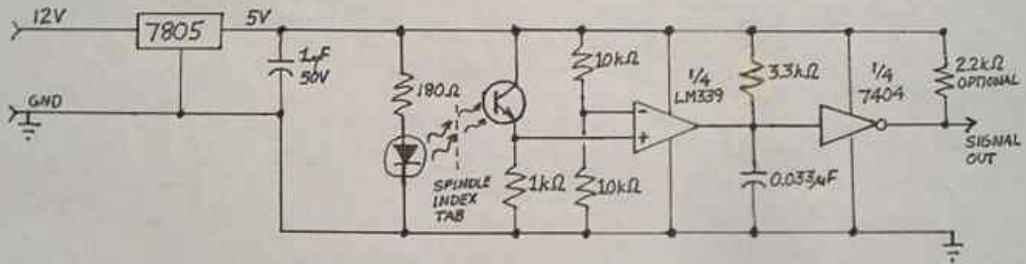


SPINDLE ENCODER CIRCUIT

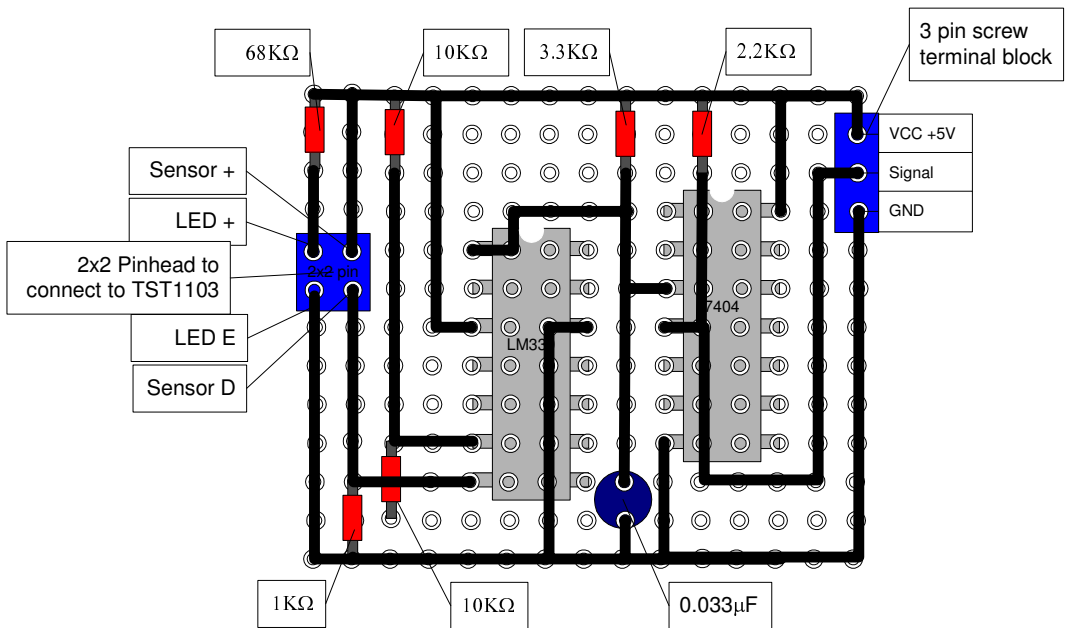

LED P/N 276-143 (RS)

XSISTOR P/N 276-145 (RS)



Lay out of Dave's encoder circuit.

Viewed from above components - Solder traces on backside. I used thin wire and put a spot of solder on each dot crossed.

10KΩ resistor crosses/staddles a trace

I used a standard paper based prototyping board with copper film around holes.

The sensor used was a TCST1103 mounted remotely.

I didn't use the 7805 and cap as my controller had 5V VCC available.